ECE320: Fields and Waves
Lab 1 Report: Waves on Transmission Lines

Alp Tarım, Pranshu Malik

September 30, 2019

1 Introduction

This assignment was about exploring the characteristics of transmission lines (abbrv. T.L.), studying voltage and current propagation along the T.L.s, as well as depedance on loads.

Introduction to the lab and its purpose. The following is the reflection coefficient for a transmission line

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

2 Determining the Characteristic Impedance, Z_0

// TODO: Ask prof about 3.2 question 1. Wording unclear

We changed the variable load on the switch box, until we saw no reflection. This was at $Z_L = 50\Omega$ which is also equal to the charactertic impedance since we know that the reflections nullify when $Z_L = Z_0$. The corresponding waveform measured at the generator input (channel 1) and the transmission line input (channel 2) is also shown in Figure 1.

Figure 1: Transmission line terminated with load equal to Z_0

3 Determining Z_0 using $\frac{v_1(t,0)}{i_1(t,0)}$

As seen in the picture the voltage at v_g is 154mV and v_1 is equal to 51mV. Assuming the resistance in between is 100Ω $i_l = \frac{0.154 - 0.051}{100} = 1.03 * 10^{-}3$A. Which means $Z_0 = \frac{v_1}{i_l} = \frac{0.051}{1.03*10^{-}3} = 49.51\Omega$ 50Ω

4   Observation of Travelling Waves

We know that the phase velocity of an electromagentic wave in space with magnetic permeability, μ, and electric permittivitty, ϵ is given by:

$$v_p = \frac{1}{\sqrt{\mu\epsilon}}$$

5   Conclusion

Lorem ipsum dolor sit amet, consectetur adipisicing elit, sed do eiusmod tempor incididunt ut labore et dolore magna aliqua. Ut enim ad minim veniam, quis nostrud exercitation ullamco laboris nisi ut aliquip ex ea commodo consequat. Duis aute irure dolor in reprehenderit in voluptate velit esse cillum dolore eu fugiat nulla pariatur.