ECE320: Fields and Waves

Lab 1 Report: Waves on Transmission Lines

Alp Tarım, Pranshu Malik

October 4, 2019

1 Introduction

This laboratory focused on investigating the characteristics of transmission lines, studying voltage and current propagation along them, as well as its depedance on the nature of load impedance.

2 Determining the Characteristic Impedance, Z_0

We varied the load on the switch box until we saw little or no traces of reflected waves. This was at $Z_L = 50\Omega$ which is also equal to the charactertic impedance since we know that the reflections nullify when $Z_L = Z_0$. The corresponding waveforms captured at the generator input (channel 1, top) and the transmission line input (channel 2, bottom) are shown in Figure 1.

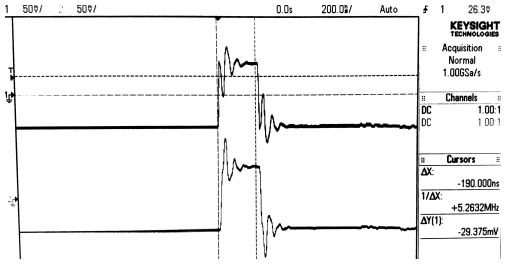

Figure 1: Transmission line terminated with load equal to Z_0

3 Determining Z_0 using $\frac{\tilde{V}^+(z=0)}{\tilde{I}^+(z=0)}$

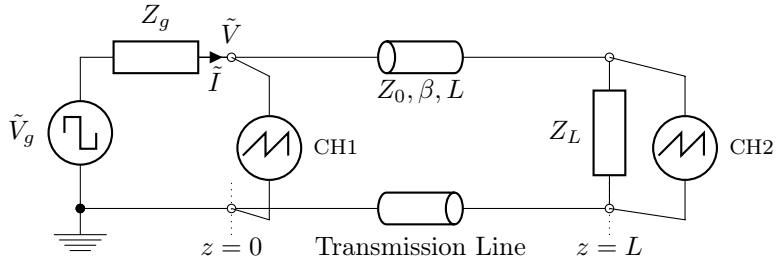

Figure 2: Laborartory setup for studying characteristcs of tranmission lines

As seen in the picture the voltage at v_g is 154mV and v_1 is equal to 51mV. Assuming the resistance in between is 100Ω $i_l = \frac{0.154-0.051}{100} = 1.03 * 10^-3$A. Which means $Z_0 = \frac{v_1}{i_l} = \frac{0.051}{1.03*10^-3} = 49.51\Omega$ 50Ω

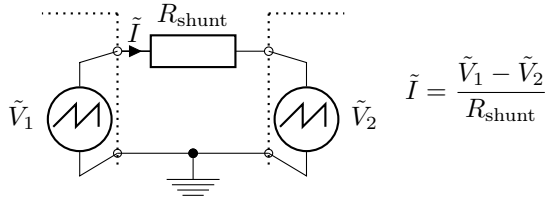

Figure 3: Estimating input current through a shunt resistance

Thus, we can see something there.

4 Observation of Travelling Waves

We know that the phase velocity of an electromagentic wave in space with magnetic permeability, μ, and electric permittivitty, ϵ is given by:

$$v_p = \frac{1}{\sqrt{\mu\epsilon}}$$

5 Observation of Travelling Waves

Testig data: voltage division.

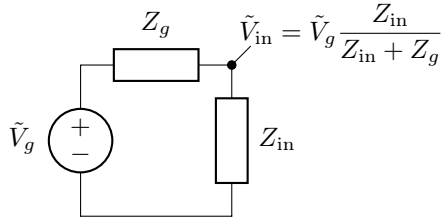

Figure 4: Circuit setup

We know that the impedance changes.

$$Z_{\text{in}} = Z_0 \frac{1 + \Gamma_d}{1 - \Gamma_d} = Z_0 \frac{Z_0 + jZ_L \tan \beta L}{Z_L + jZ_0 \tan \beta L}$$

6 Conclusion

Lorem ipsum dolor sit amet, consectetur adipisicing elit, sed do eiusmod tempor incididunt ut labore et dolore magna aliqua. Ut enim ad minim veniam, quis nostrud exercitation ullamco laboris nisi ut aliquip ex ea commodo consequat. Duis aute irure dolor in reprehenderit in voluptate velit esse cillum dolore eu fugiat nulla pariatur.

7 Notes

All pictures taken during the lab were post-processed in a batch using a custom script that bit-wise inverted the pixels and the thresholded to produce a binarized image. No adjustments or modifications were made to the readings, for which the oscilloscope's measurements are also shown alongside the waveforms. All work can be found at `github.com/pranshumalik14/ece320-labs`.